

PROJECT REPORT
BTECH 3rd Year

ANALOG CIRCUITS

Course: EE301



Course Instructor: Dr. Mahendra Sakare

Teaching Assistant: Puneeth Singh, Mayank Kumar Singh,

Upendra Chichhula, Hirens Mehra

Department of Electrical Engineering

Submitted By:-

Kotni Revathi Devi-2020EEB1179

AIM: To design beta multiplier, cascode current mirror and cascode amplifier in ltspice and magic.

CALCULATIONS:

→ For 180nm:

Let the assumed current, $I_d = 10\mu A$ and unity gain frequency, $f_u = 3MHz$

Required gain = 20V/V

$$f_u = \frac{1}{2 \times \pi \times R_{out} \times C}$$

$$R_{out} = \frac{1}{2 \times \pi \times f_u \times C}$$

$$R_{out} = \frac{1}{2 \times \pi \times 3M \times 1p}$$

$$R_{out} = 53051.6476\Omega$$

$$A_v = g_m \times R_{out} \Rightarrow g_m = \frac{A_v}{R_{out}} = \frac{20}{53051.6476} \Rightarrow g_m = 3.14 \times 10^{-4}$$

$$g_m = \sqrt{2 \times I_d \times u_n \times C_{ox} \times \frac{W}{L}} = \sqrt{2 \times 10\mu \times 270\mu \times \frac{W}{L}}$$

$$314.159 = 18.277 \sqrt{\frac{W}{L}}$$

$$\bullet \left(\frac{W}{L}\right)_n = 18.277$$

V_g, V_s, V_{thp} be the gate voltage of 1st pmos in cascode amplifier,

$$\Rightarrow V_g = V_{bias1}$$

From cascode current mirror, $V_{bias1} = 1.08V$

$$V_s = 1.8V, V_{thp} = 0.3906$$

$$I_d = 0.5 \times u_p \times C_{ox} \times \frac{W}{L} \times (V_{gs} - V_{thp})^2$$

$$10\mu = 0.5 \times 45\mu \times \frac{W}{L} \times 0.1085 \Rightarrow \frac{W}{L} = 4.096$$

$$\bullet \left(\frac{W}{L}\right)_p = 4.096$$

→ For 22nm:

Let the assumed current, $I_d = 8\mu A$ and unity gain frequency, $f_u = 1MHz$

Required gain = 20V/V

$$f_u = \frac{1}{2 \times \pi \times R_{out} \times C}$$

$$R_{out} = \frac{1}{2 \times \pi \times f_u \times C}$$

$$R_{out} = \frac{1}{2 \times \pi \times 1M \times 1p}$$

$$R_{out} = 159154.94\Omega$$

$$A_v = g_m \times R_{out} \Rightarrow g_m = \frac{A_v}{R_{out}} = \frac{20}{159154.94} \Rightarrow g_m = 12 \times 10^{-5}$$

$$g_m = \sqrt{2 \times I_d \times u_n \times C_{ox} \times \frac{W}{L}} \Rightarrow 12 \times 10^{-5} = \sqrt{2 \times 8\mu \times 120\mu \times \frac{W}{L}}$$

$$120 = 43.8178 \sqrt{\frac{W}{L}}$$

$$\bullet \left(\frac{W}{L}\right)_n = 7.5$$

V_g, V_s, V_{thp} be the gate voltage of 1st pmos in cascode amplifier,

$$\Rightarrow V_g = V_{bias1}$$

From cascode current mirror, $V_{bias1} = 0.2481V$

$$V_s = 0.8V, V_{thp} = 0.44$$

$$I_d = 0.5 \times u_p \times C_{ox} \times \frac{W}{L} \times (V_{gs} - V_{thp})^2$$

$$4\mu = 0.5 \times 55\mu \times \frac{W}{L} \times 0.012544 \Rightarrow \frac{W}{L} = 11.59554$$

- $\left(\frac{W}{L}\right)_p = 11.59554$

INPUTS OF CASCODE AMPLIFIER

→ For 180nm

For nmos to be in saturation region,

$$V_{ds} \geq V_{gs} - V_{thn}$$

Let us assume $V_{dsat} = 200m$

- For M4,
 $200m \geq V_s - 0.5, \Rightarrow V_s \leq 0.7$
- For M3,
 $200m \geq V_{bias3} - 0.2 - 0.5$
 $V_{bias3} \leq 0.7$


For pmos to be in saturation region,

$$V_{ds} \leq V_{gs} - V_{thp}$$

- For M2,
 $-200m \leq V_{bias2} - 1.6 + 0.3906$
 $V_{bias2} \geq 1.0094$
- For M1,
 $-200m \leq V_{bias1} - 1.8 + 0.3906$
 $V_{bias1} \geq 1.2094$

Spice Values:

- $V_{bias1} = 1.08V$

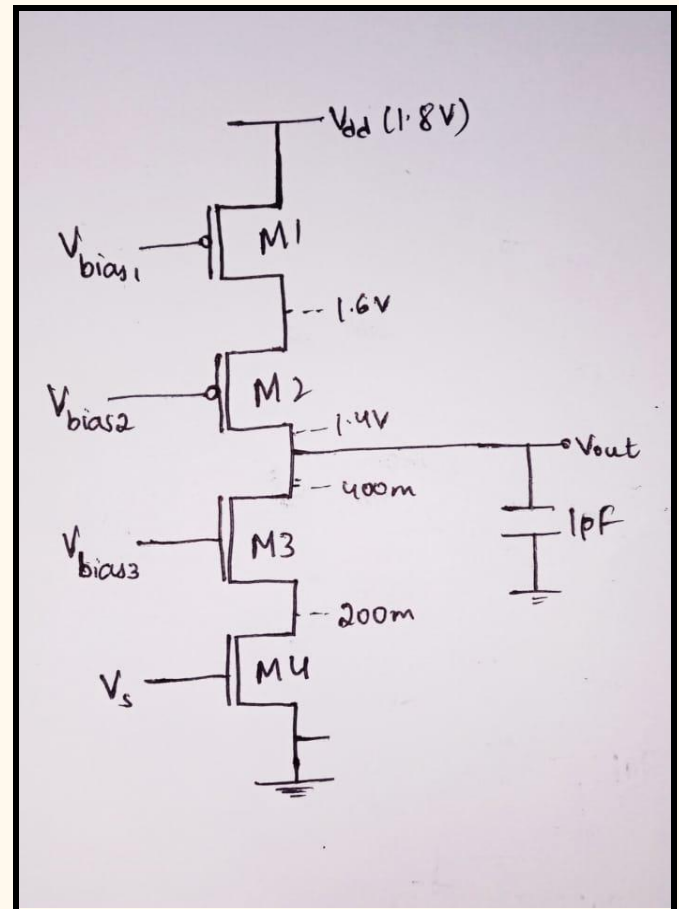

- $V_{bias2} = 941.2\text{mV}$
- $V_{bias3} = 649.62\text{mV}$
- V_s taken is 500m

→ For 22nm

For nmos to be in saturation region,

$$V_{ds} \geq V_{gs} - V_{thn}$$

Let us assume $V_{dsat} = 200\text{m}$

- For M4,
 $200\text{m} \geq V_s - 0.5, \Rightarrow V_s \leq 0.7$
- For M3,
 $200\text{m} \geq V_{bias3} - 0.2 - 0.5$
 $V_{bias3} \leq 0.7$


For pmos to be in saturation region,

$$V_{ds} \leq V_{gs} - V_{thp}$$

- For M2,
 $-200\text{m} \leq V_{bias2} - 0.6 + 0.46$
 $V_{bias2} \geq -0.06$
- For M1,
 $-200\text{m} \leq V_{bias1} - 0.8 + 0.3906$
 $V_{bias1} \geq 0.14$

Spice Values:


- $V_{bias1} = 248.126\text{mV}$

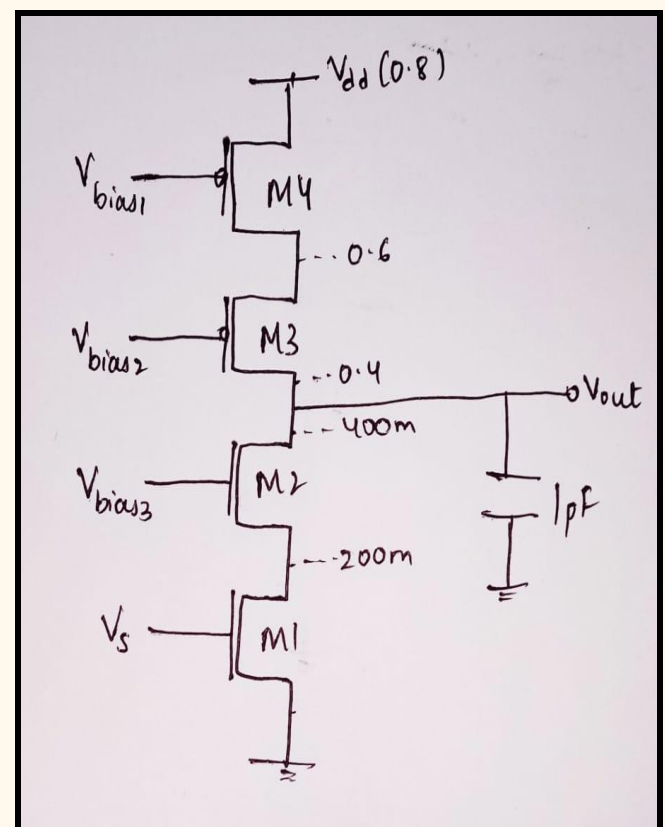


BETA MULTIPLIER

The circuit diagram illustrates a BETA MULTIPLIER. It is powered by a 1.8V VDD source (V1). The circuit consists of several MOSFETs (M1 through M12) and a resistor (R1). The PMOS network (CMOSP) includes M1, M2, M3, M4, and M11. The NMOS network (CMOSN) includes M5, M6, M7, M8, M9, M10, and M12. The output node is connected to VDD through M11 and to ground through M10. A 5.5k resistor (R1) is connected between the output node and ground. The circuit is biased by Vbiasb. The output is labeled 'Vout'.

CASCODE CURRENT MIRROR

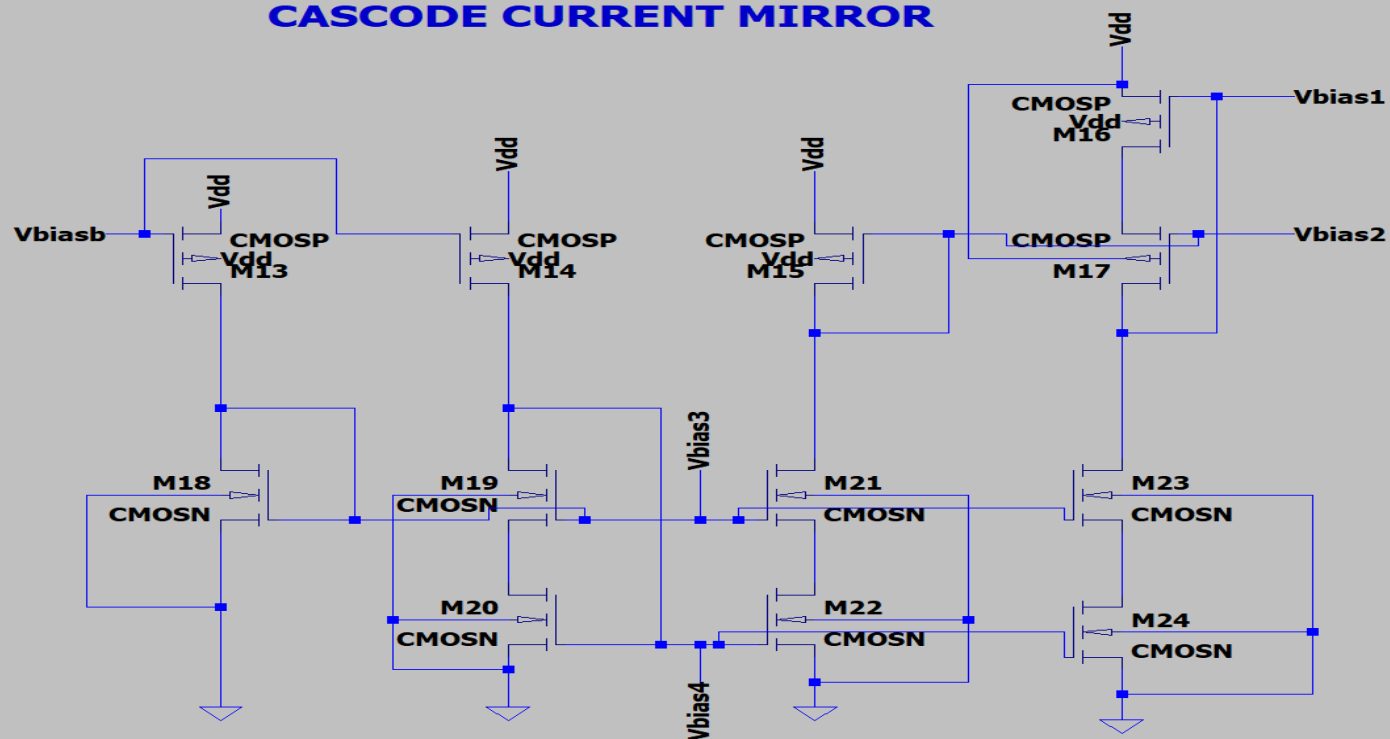

CASCODE CURRENT AMPLIFIER

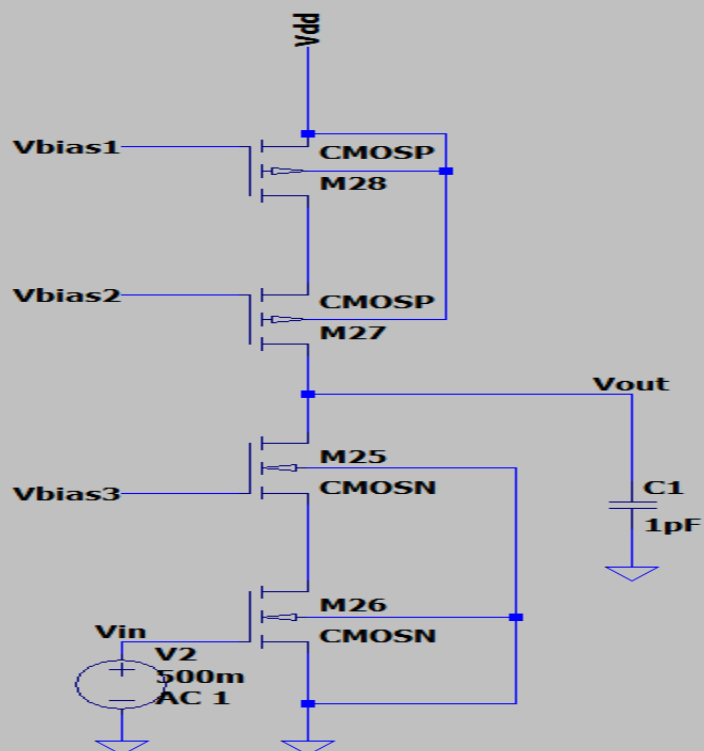

LAYOUT

Cascode Current Mirror

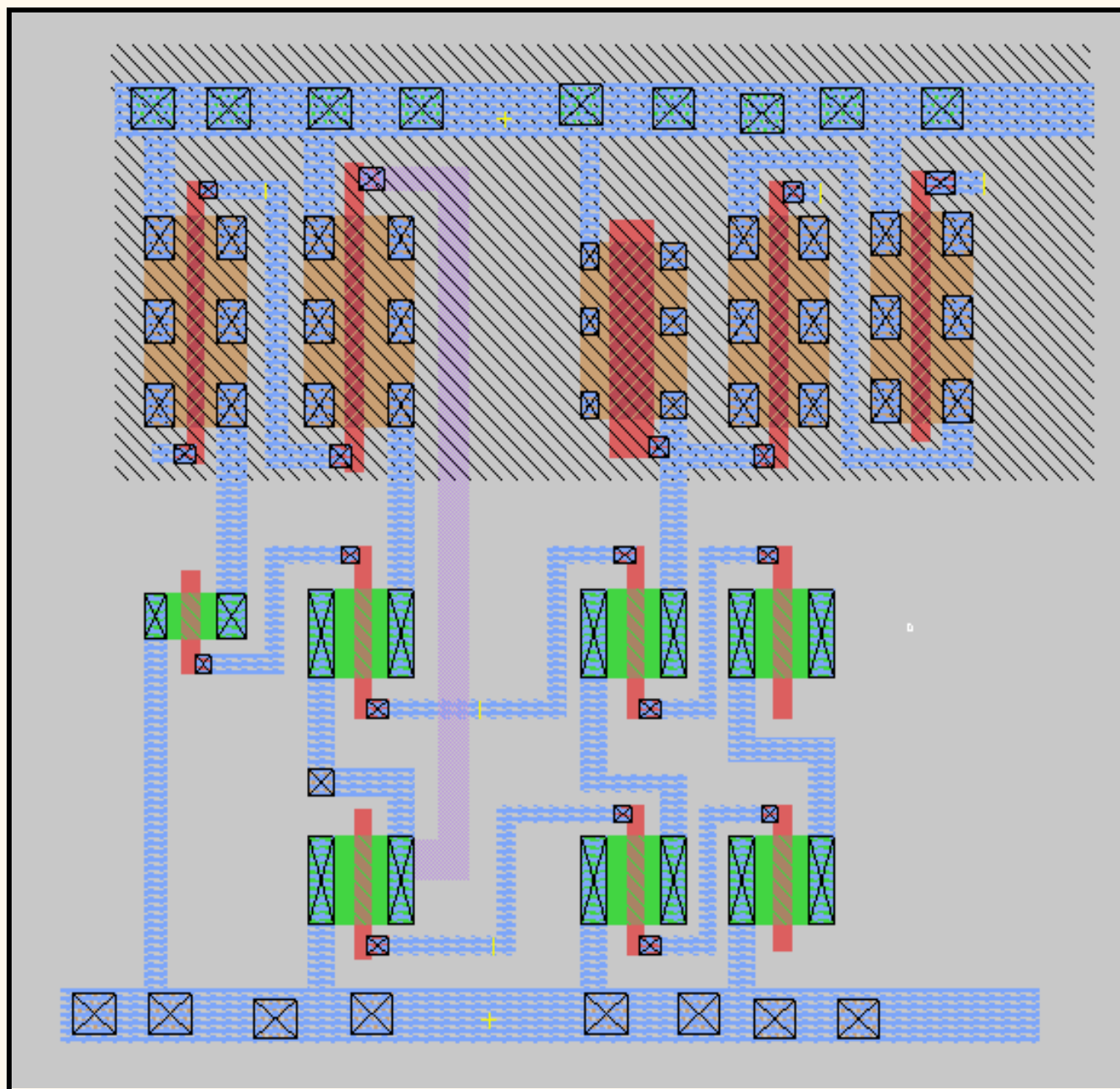


Fig: Cascode Current Mirror Layout

Cascode Amplifier

 


Fig: Cascode Amplifier

OBSERVATIONS:

Ltspice Plots:-

For 180nm:

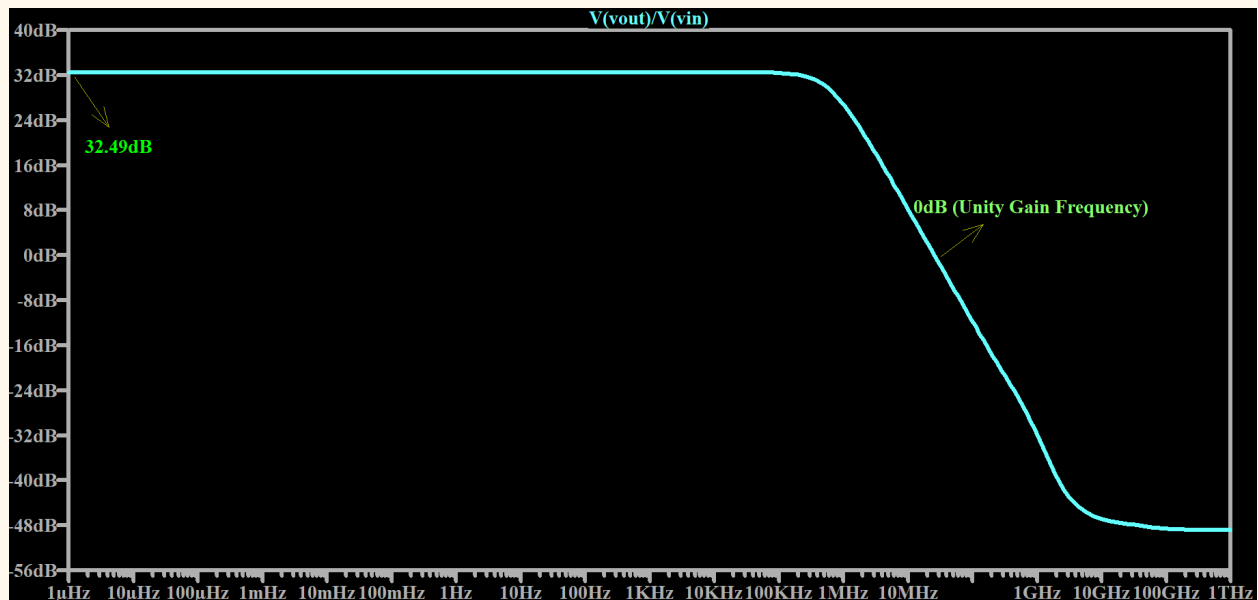


Fig: Frequency Response

 


Fig: Vbias Values

 


Fig: Sine Input

For 22nm:

 


Fig: Frequency Response

 


Fig: Vbias Values

 


Fig: Sine Input

TABLES:

Technology File	Assumed Values		Spice Values		
	Unity Gain Frequency	Current (microamps)	Unity Gain Frequency	Current (microamps)	Gain (dB)
180nm	10MHz	10	25MHz	8.92	32.49
22nm	1MHz	4	2.78MHz	5.84	26.26

Technology File	Calculated Values			Spice Values		
	gm	$\frac{W}{L}_{nmos}$	$\frac{W}{L}_{pmos}$	gm	$\frac{W}{L}_{nmos}$	$\frac{W}{L}_{pmos}$
180nm	3.14e-04	18.277	4.096	1.7e-04	15	5
22nm	12e-05	7.5	11.59	4.59e-05	5	9.39

REQUIRED SPECIFICATIONS:

- Required gain is $20V/V = 20\log(20) = 26.02\text{dB}$, hence simulated gain should be atleast 26.02dB. Gain is 32.49dB and 26.26dB for 180nm and 22nm respectively.
 - Power dissipation $\leq 5\text{mW}$. From simulated data $16\mu\text{W}$ and $4\mu\text{W}$ for 180nm and 22nm respectively.
 - Unity Gain Frequency must be greater than 500KHz. It is 25MHz and 2.78MHz for 180nm and 22nm respectively.
 - Frequency response must be a low pass filter.
- Hence required specifications are satisfied.

CONCLUSION: Beta Multiplier, Cascode Current Mirror and Cascode Amplifier are simulated in ltspice and magic software. Practical calculations are almost appropriate to ltspice values. Different analyses are made and understood. It's also visible from the observation tables that the assumed, calculated and spice values of different parameters are approximately in the same ranges, which verifies that the simulations and practical calculations are almost matched with each other.
